

EECS240 – Spring 2010

Lecture 22: Offset Cancellation



Elad Alon
Dept. of EECS


Offset Cancellation Overview

- Two main ideas/approaches
- Modulate and/or filter offset so that it is outside of signal band
 - CDS (auto-zeroing)
 - Chopping (synch. detection, DEM)
- Inject a DC signal that opposes the offset
 - Trimming
 - Often digitally controlled (especially for comparators)

Filtering/Modulating Offset

- **General idea:**
 - Put elements around the amplifier that treat offset differently than signal
- **CDS:**
 - Configure amplifier so that offset is (approx.) differentiated
- **Chopping:**
 - Modulate offset to frequencies beyond signal band, then filter it out

CDS #1: Output Offset Cancellation

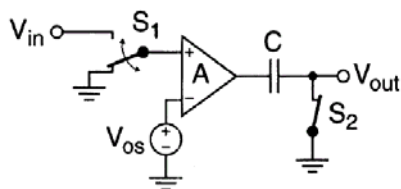

Phase 1 :

$$V_C = -AV_{os}$$


Phase 2 :

$$\begin{aligned} V_{out} &= A(V_{in} - V_{os}) - V_C \\ &= AV_{in} \end{aligned}$$

- **Relatively insensitive to switch errors**
 - Storing amplified offset
- **But, what happens if gain is large?**

CDS #2: Input Offset Cancellation


Multistage Cancellation

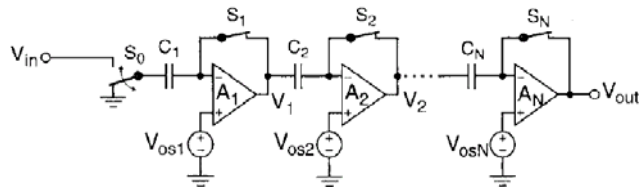

- **Open switches left to right**
 - Errors from $S_1 \dots S_{N-1}$ cancelled by final stage
- **Application: continuous time comparators**

Auxiliary Amplifier Offset Cancellation


Aux. Amplifier Example

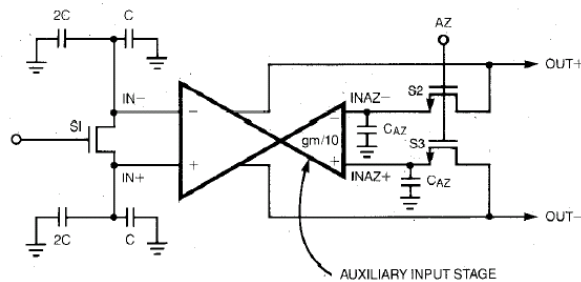

H. Ohara, H. X. Ngo, M. J. Armstrong, C. F. Rahim, and P. R. Gray, "A CMOS programmable self-calibrating 13-bit eight-channel data acquisition peripheral," *IEEE Journal of Solid-State Circuits*, vol. 22, pp. 930 - 938, December 1987.

Aux. Amplifier Implementation

CDS and Flicker Noise

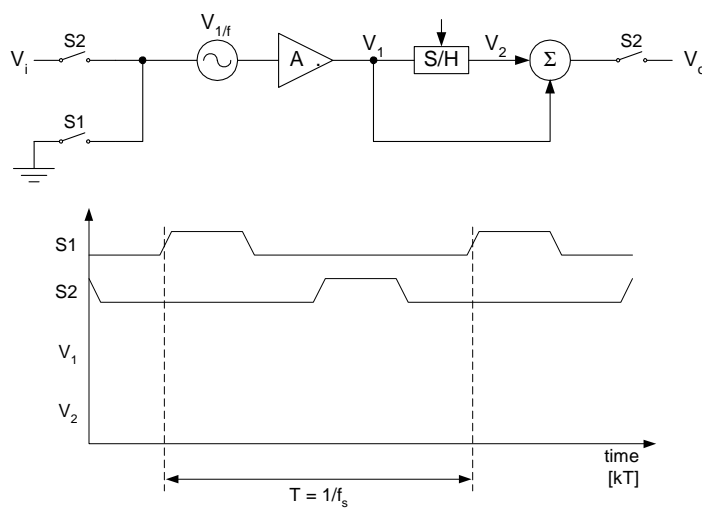

Flicker Noise Analysis

$$V_o(kT) = A \left\{ \underbrace{V_i(kT)}_{\text{signal}} + \underbrace{V_{1/f}(kT) - V_{1/f}\left(kT - \frac{T}{2}\right)}_{\text{input referred error } V_{nieq}} \right\}$$

Laplace Transform

Delay by $t_d \rightarrow e^{-st_d}$


$$V_{nieq}(s) = V_{1/f}(s) \underbrace{\left\{ 1 - e^{-\frac{sT}{2}} \right\}}_{H_n(s)}$$

Flicker Noise Frequency Response

$$\begin{aligned} H_n(s) &= 1 - e^{-\frac{sT}{2}} \\ &= 1 - e^{-j\omega\frac{T}{2}} \\ &= 1 - \cos\frac{\omega T}{2} + j \sin\frac{\omega T}{2} \end{aligned} \quad \begin{aligned} |H_n(s)|_{s \rightarrow j\omega}^2 &= \left(1 - \cos\frac{\omega T}{2}\right)^2 + \left(\sin\frac{\omega T}{2}\right)^2 \\ &= 1 - 2\cos\frac{\omega T}{2} + \underbrace{\cos^2\frac{\omega T}{2} + \sin^2\frac{\omega T}{2}}_1 \\ &= 2\left(1 - \cos\frac{\omega T}{2}\right) \\ &= 4\sin^2\frac{\omega T}{4} \end{aligned}$$

$$|H_n(s)|_{s \rightarrow j\omega} = \left| 2 \sin\frac{\omega T}{4} \right| = \left| 2 \sin\frac{\pi f}{2f_s} \right|$$


Flicker Noise Spectrum

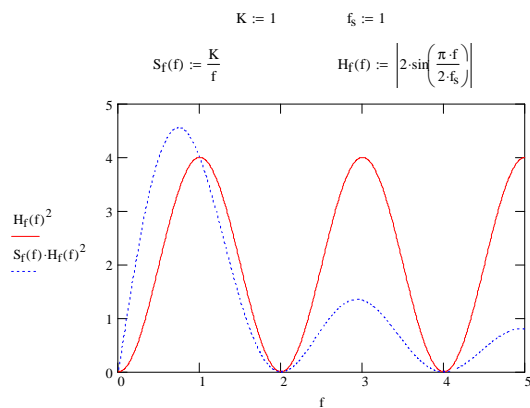

- Flicker noise is differentiated
 - As is thermal noise
- Noise removed at low freq.
 - But amplified at “high” freq.
- Noise above $f_s/2$ folds to baseband

Chopping

Nested Chopper Amplifier

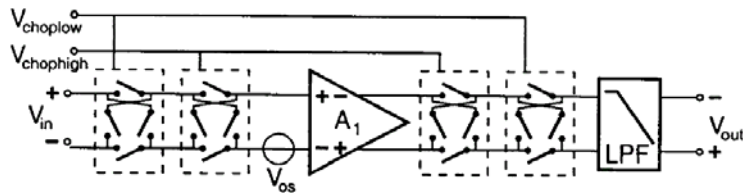

- Inner chopper at high freq. to remove $1/f$ noise
- Outer chopper at low frequency to minimize “spiking” and remove residual offset from inner chopper.

Offset Trimming

Digital Trimming

Comparator Trimming

Trim Implementation Issues

- **Infinite number of ways to introduce digitally controlled offset**
 - People have tried just about all of them
- **Key issues:**
 - Power overhead
 - Circuit Imbalance
 - Effective resolution
 - Area overhead

Comparator Trim Schemes

Pre-Amp Trim

Pre-Amp Trim
