


EECS240 – Spring 2010

Lecture 9: Amplifiers



Elad Alon
Dept. of EECS

How about Capacitive Feedback?

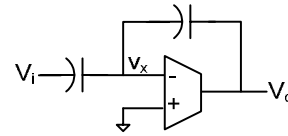

- **At low frequency:**
 - No loading from feedback network ($|Z_f| = \infty$)
- **Gain drops at high frequency**
 - But this happens in all amplifiers
- **Does this really work?**
 - Hint: what happens if you simulate this in SPICE?


EECS240

Lecture 9

4


OpAmps and OTAs

OpAmp

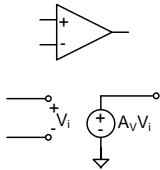

- High voltage gain, high input impedance
- Voltage source output (low impedance)

OTA

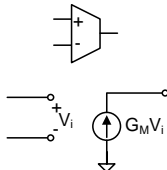


- High “voltage” gain, high input impedance
- Current source output (high impedance)

EECS240

Lecture 9

2

Capacitive Feedback cont'd

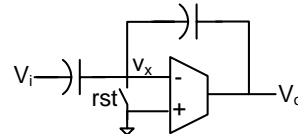


- Charge on v_x is undefined – needs to be reset to known value
- Can we just do this once at start-up?
 - Depends how long you want to use the amplifier...
- Usually do this “reset” every cycle
 - Why each cycle instead of only once every N cycles?

EECS240


Lecture 9

5

Resistive Feedback

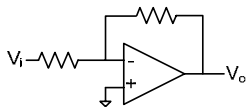

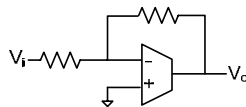- Open-loop gain: ∞
- (Independent of R_f)




- Open-loop gain: $G_m R_f$
 - Feedback loads the OTA
- How about large R_f ?
 - Lots of area, parasitic poles
- Need a different solution...

EECS240

Lecture 9

3

Switched-Capacitor Gain Stage

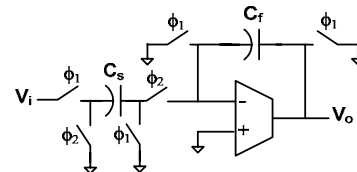

- Many possible topologies – one example shown here
- Clocks generally non-overlapping


EECS240

Lecture 9


6

SC Gain Stage Phases

- Phase 1:

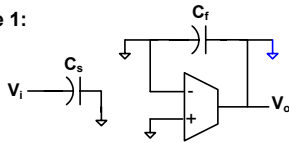

- Phase 2:

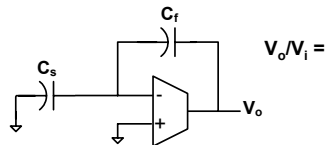


EECS240

Lecture 9

7

Opamp vs. OTA Noise

OpAmp

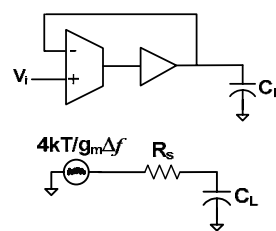


$$V_{o,n}^2 = \frac{4k_B T}{g_m} \frac{1}{4R_s C_L} = \frac{k_B T}{C_L} \frac{R_n}{R_s}$$

EECS240

Lecture 9

10

OTA

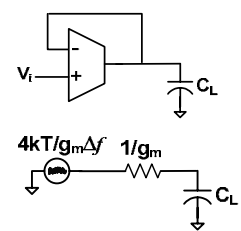

$$V_{o,n}^2 = \frac{k_B T}{C_L}$$

SC Gain Stage Waveforms

EECS240

Lecture 9

8


SC Gain Stage Noise

EECS240

Lecture 9

11

Opamp vs. OTA Revisited

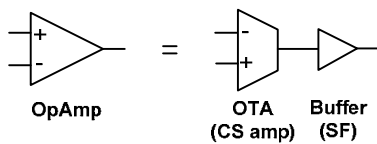

EECS240

Lecture 9

9