

EECS240 – Spring 2010


Lecture 10: Single-Ended and Differential OTAs



Elad Alon
Dept. of EECS

Simplest Single-Ended OTA

DC Input/Output, Gain

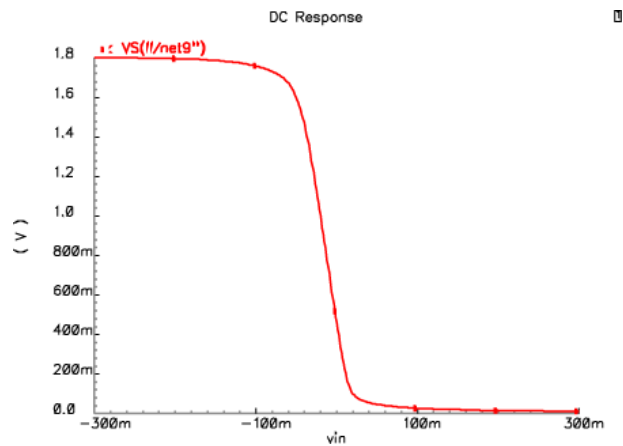

Gain, Output Range


- **Small Signal:**

$$a_{vo} = \frac{dV_{out}}{dV_{in}}$$


- **Large Signal:**

$$A_{vo} = \frac{V_{out} - V_{out_o}}{V_{in} - V_{in_o}}$$

Frequency Response

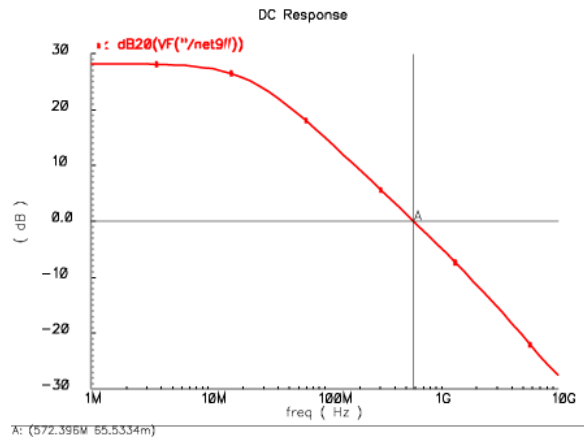


Noise

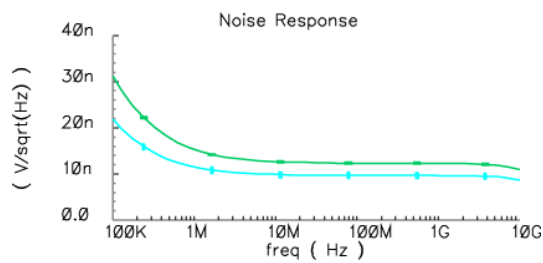


$$\begin{aligned} \frac{\overline{v_{ieq}^2}}{\Delta f} &= 4k_B T \gamma \frac{1}{g_{m1}^2} (g_{m1} + g_{m2}) \\ &= 4k_B T \gamma \frac{1}{g_{m1}} \left(1 + \frac{g_{m2}}{g_{m1}} \right) \\ &= 4k_B T \gamma \frac{1}{g_{m1}} \underbrace{\left(1 + \frac{V_1^*}{V_2^*} \right)}_{n_f} \end{aligned}$$

Differential Input?

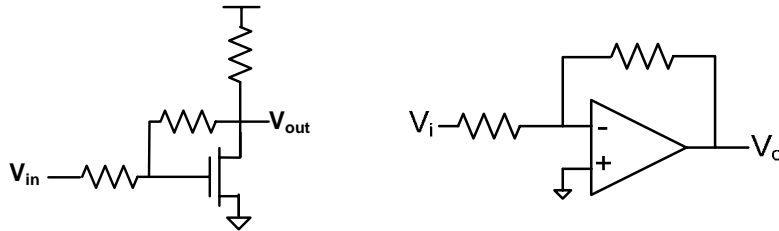


- **Why use a differential input?**
 - Diff. version has extra device(s) – more power, noise, etc.
- **Real reason is systematic offset**
 - All voltages are relative
- **Inherent asymmetry to get single-ended V_{out}**
 - “common-mode” sensitivity

Fully Differential Circuits

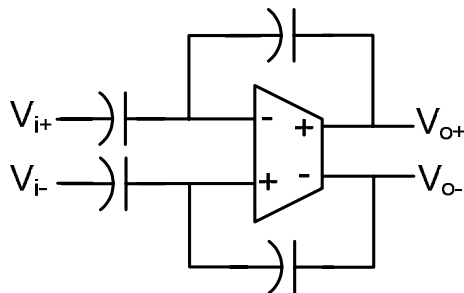

- **Fully differential circuits: complete symmetry**
 - $V_{id} = V_{i+} - V_{i-}$ $V_{ic} = (V_{i+} + V_{i-})/2$
 - $V_{od} = V_{o+} - V_{o-}$ $V_{oc} = (V_{o+} + V_{o-})/2$
- **Still need to be careful with common mode**

Fully Differential Amplifier Gains

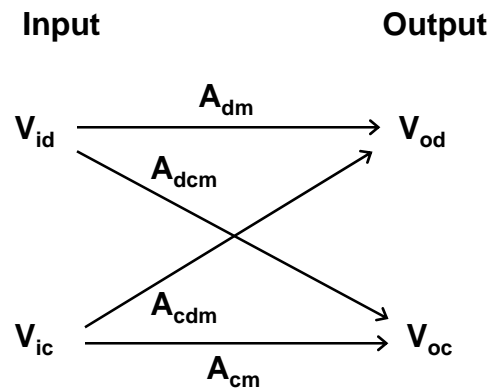


PSRR, CMRR, ...

$$\begin{aligned}
 A_{dm} &= \frac{v_{od}}{v_{id}} \rightarrow \infty & A_{VDD} &= \frac{v_{od}}{v_{DD}} \rightarrow 0 & CMRR &= \left| \frac{A_{dm}}{A_{cdm}} \right| \rightarrow \infty \\
 A_{cm} &= \frac{v_{oc}}{v_{ic}} \rightarrow 0 & A_{VSS} &= \frac{v_{od}}{v_{SS}} \rightarrow 0 & PSRR_{VDD} &= \left| \frac{A_{dm}}{A_{VDD}} \right| \rightarrow \infty \\
 A_{cdm} &= \frac{v_{od}}{v_{ic}} \rightarrow 0 & & & PSRR_{VSS} &= \left| \frac{A_{dm}}{A_{VSS}} \right| \rightarrow \infty
 \end{aligned}$$

- **All “terminals” are inputs**
 - May not be a node in the circuit – could be e.g. temperature
- **Typical metrics: CMRR, PSRR**
 - Careful with how you use these

CMRR Example

Differential Input Stage Options

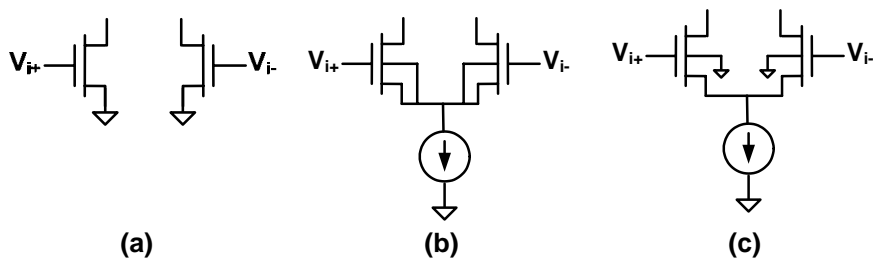

PSRR Example

Baluns
