


EECS240 – Spring 2010

Lecture 13: Settling



Elad Alon
Dept. of EECS

Static Error

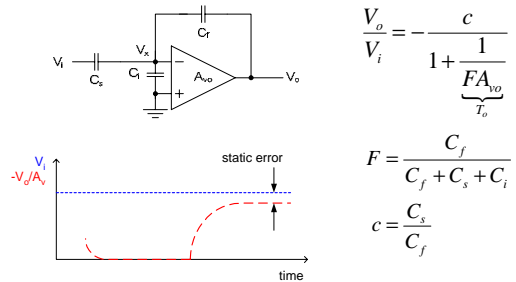


EECS240

Lecture 13

4

Settling

- Why interested in settling?
 - Oscilloscope: track input waveform without ringing
 - ADC (switched-cap amplifier): gain a signal up by a precise amount within T_{sample}

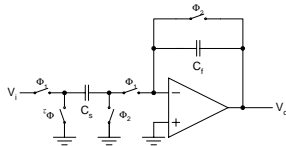

EECS240

Lecture 13

2

Static Error (cont.)

$$\frac{V_o}{V_i} = -\frac{c}{1 + \frac{1}{FA_{vo}}} \approx -c \left(1 - \frac{1}{FA_{vo}} \right)$$

relative error

- **Example:**
 - Closed loop gain: $c = -4$, $C_f = 1\text{pF}$, $C_s = 4\text{pF}$, $C_i = 1\text{pF}$
 - $F = 1/6$ (C_i hurts!)
- Error specification: $<0.1\%$
 - $FA_{vo} > 1000$
 - $A_{vo} > 6000$ over output range


EECS240

Lecture 13

5

Step Response

- Two types of settling “errors”:
 - Static
 - Finite gain, capacitor mismatch
 - Dynamic
 - Takes time to reach final value

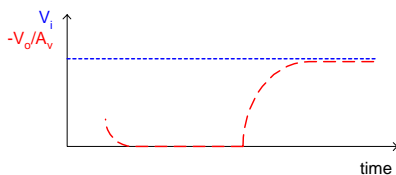

EECS240

Lecture 13

3

Dynamic Errors

- Many possible dynamic effects that impact settling error:
 - Finite bandwidth
 - Feedforward zero
 - Non-dominant poles
 - Doublets
 - Slewing
- Approximate analysis approach:
 - Decompose each error source, isolate interactions
 - Add all errors together


EECS240

Lecture 13

6

Single Time Constant Linear Settling

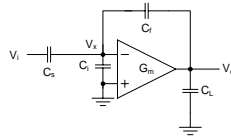- For dynamic settling (and for $T_0 \gg 1$), can generally ignore r_o



$$\frac{V_o}{V_i} = -c \frac{1 - s \frac{C_f}{G_m}}{1 + s \frac{C_L + (1-F)C_f}{FG_m}}$$

Case 1: $|p/z| \ll 1$

$$v_{o,step}(t) \equiv \underbrace{-V_{step}c}_{\text{ideal response}} \left[1 - e^{-t/\tau} \right]$$

Relative settling error:

$$\varepsilon = \frac{v_o(t \rightarrow \infty) - v_o(t = t_s)}{v_o(t \rightarrow \infty)} = e^{-t_s/\tau}$$

$$\frac{t_s}{\tau} = -\ln \varepsilon$$

- Easiest number to remember: 2.3τ per decade
- Example: 1% settling, 4.6ns clock cycle: $\tau = 1\text{ns}$
- $C_{L,eff}$ usually set by noise – use settling to determine required g_m

Time Domain Step Response

Frequency domain:

Time domain:

$$V_{o,step} = -c \frac{1 + s/z}{1 + s/p} \frac{V_{step}}{s}$$

Case 2: $|p/z|$ not negligible

$$v_{o,step}(t) \equiv \underbrace{-V_{step}c}_{\text{ideal response}} \left[1 - \left(1 - \frac{p}{z} \right) e^{-t/\tau} \right]$$

Relative settling error:

$$\varepsilon = \frac{v_o(t \rightarrow \infty) - v_o(t = t_s)}{v_o(t \rightarrow \infty)} = \left(1 - \frac{p}{z} \right) e^{-t_s/\tau}$$

$$\frac{t_s}{\tau} = -\ln \left(\frac{\varepsilon}{1 + F C_f / C_{Leff}} \right)$$

- Example:**
 - $c = 0.25$, $C_f = 1\text{pF}$, $C_s = 250\text{fF}$, $C_i = 250\text{fF}$, $C_L = 1\text{pF}$
 - $F = 0.67$, $C_{L,eff} = 1.33\text{pF}$
- $\varepsilon = 0.1\%$:
 - t_s (no feedforward) = 6.9τ
 - t_s (with feedforward) = $-\ln[1e-3/(1+0.67*0.75)] = 7.3\tau$

Time Domain Step Response

Frequency domain:

Time domain:
(inverse Laplace transform)

input step:

$$V_{i,step} = \frac{V_{step}}{s}$$

output step:

$$V_{o,step} = -c \frac{1 + s/z}{1 + s/p} V_{i,step}$$

$$= -c \frac{1 + s/z}{1 + s/p} \frac{V_{step}}{s}$$

$$v_{o,step}(t) = \underbrace{-V_{step}c}_{\text{ideal response}} \left[1 - \underbrace{\left(1 - \frac{p}{z} \right)}_{\substack{\text{initial error} \\ \text{(feedforward)}}} e^{-pt} \right]$$

exponentially decaying error

Non-Dominant Pole

- Ignore feed-forward zero for simplicity
 - (Just increases final swing by $1 + F C_f / C_{Leff}$)

$$H(s) = \frac{V_o}{V_{in}} = -c \frac{1}{1 + s \frac{C_{Leff}}{FG_m}}$$


- Model for non-dominant pole:

$$G_m(s) = \frac{G_{m0}}{1 + s/p_2}$$

$$p_2 = K \omega_u$$

ω_u is unity gain bandwidth of $T(s)$

Step Response

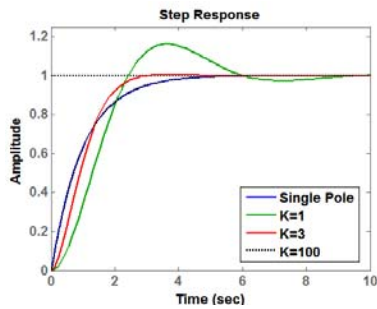


EECS240

Lecture 13

13

Non-Dominant Pole vs. ϵ

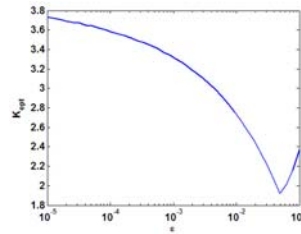

- Optimum K actually depends on required accuracy
- Still, always want to avoid $K < 2$


EECS240

Lecture 13

16

Non-Dominant Pole (cont.)

Relative error: $\epsilon = |1 - v_s(t, K)|$

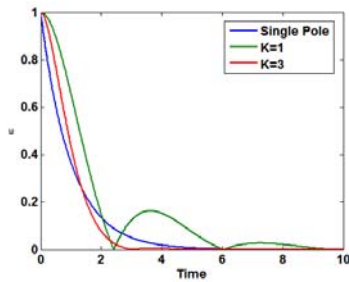

EECS240

Lecture 13

14

Doublets

- Amplifier model:

$$G_m(s) = G_{mo} \frac{1 + s/\omega_z}{1 + s/\omega_p} \quad \text{with} \quad \omega_z = \frac{\omega_L}{\alpha} \quad \omega_p = \beta\omega_{-3dB} \quad \omega_{-3dB} \text{ is bandwidth of } T(s)$$

$$\alpha = 1 + \epsilon \quad \text{with} \quad |\epsilon| \ll 1$$

- Closed-loop gain (ignore feedforward zero):

$$\frac{V_o}{V_{in}} = -c \frac{1}{1 + s \frac{C_{Leff}}{FG_m(s)}} \approx -\frac{c}{1 + s/\omega_{-3dB}} \left(\frac{1 + s/\omega_z}{1 + s/\omega_{pp}} \right) \quad \omega_{-3dB} \equiv \frac{FG_{mo}}{C_{Leff}}$$

$$\omega_{pp} \equiv \omega_p$$


EECS240

Lecture 13

17

Settling Time

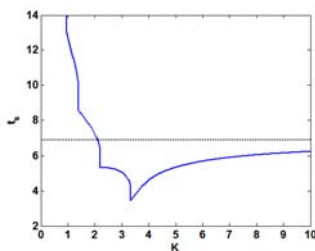Settling time: $t_s(K)$ for $\epsilon = 10^{-3}$, $\tau = 1$



- Optimum at $K=3.3$

EECS240

Lecture 13

15

Doublet Analysis

- Step response

$$v_{o,step}(t) = -cV_{step} \left(1 - Ae^{-t\omega_{-3dB}} - Be^{-t\omega_{pp}} \right)$$

$$B \approx \epsilon \frac{\beta}{(1 - \beta)^2}$$


$$A \approx 1 - B \approx 1$$

EECS240

Lecture 13

18

Doublet Example

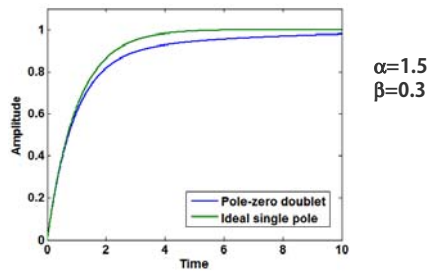

Slewing


- Transconductor ΔI vs. ΔV :
- Model for (nonlinear) slewing amplifier
 - Piecewise linear approximation:
 - Slewing with constant current, followed by
 - Linear settling exponential
 - $t_s = t_{\text{slew}} + t_{s,\text{lin}}$

Doublet Conclusions

- Case A: $\tau_2 \leq \tau_1$ i.e. $\beta \geq 1$
 - Doublet settles faster than amplifier
 - Has no impact on overall settling time
- Case B: $\tau_2 > \tau_1$
 - Doublet settles more slowly than amplifier
 - Determines overall settling time (unless ϵ within settling accuracy requirements)
- → Avoid "slow" doublets!


Slewing Analysis

- Circuit model during slewing:

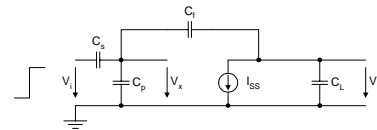

Final Note on Doublets

Slewing Analysis (cont.)

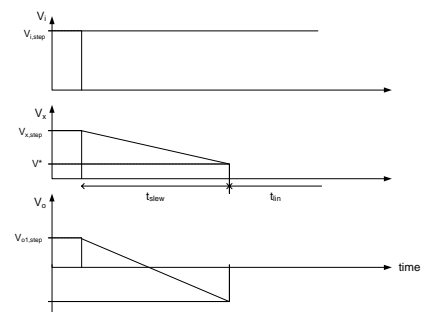

Slewing Analysis (cont.)

- Slewing period:

$$V_{x,step} = V_{i,step} \frac{C_i}{C_i + C_2} \quad \text{with} \quad C_2 = C_f + \frac{C_f C_L}{C_f + C_L}$$

$$\Delta V_x = V_{x,step} - V^* \rightarrow \Delta V_o = \frac{\Delta V_x}{F}$$

$$t_{slew} = \frac{\Delta V_o}{SR} = \frac{\Delta V_x C_{eff}}{F I_{SS}}$$

- Linear settling during final V^* of swing at V_x :

- Step during linear settling: V^*/F

- Linear settling time: $\frac{t_{s,lin}}{\tau} = -\ln\left(\varepsilon \frac{C V_{i,step} F}{V^*}\right)$