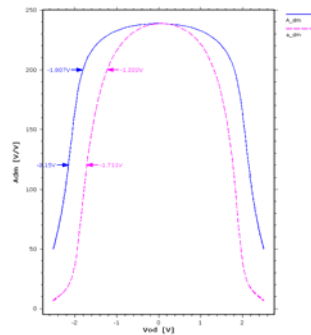


4



Low Frequency Gain, A_{dm}




EECS240

Lecture 11

7

Biasing and Parasitic Feedback

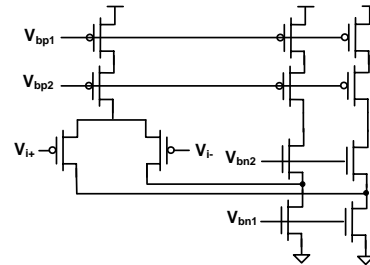


EECS240

Lecture 11

10

Output Resistance

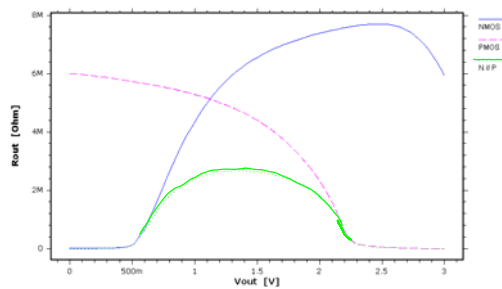


Beware of r_o imbalance between NMOS and PMOS current sources

EECS240

Lecture 11

8

Input Cascode

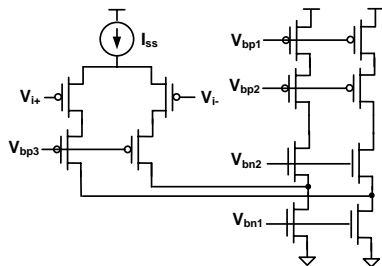

EECS240

Lecture 11

9