

EECS240 – Spring 2010

Lecture 16: Multistage Amplifiers




Elad Alon
Dept. of EECS

Why use Multi-Stage Amplifiers?

- **Single-stage amplifier:**
 - Generally have to trade between swing and gain
 - (Need cascodes and/or large V_{\min} for current sources)
- **Multi-stage amplifier:**
 - Higher gain without sacrificing swing
 - (Gain-boosted cascode is multi-stage amplifier in disguise)
- **Challenge: stability!**

Stability for Simple 2-Stage Amp

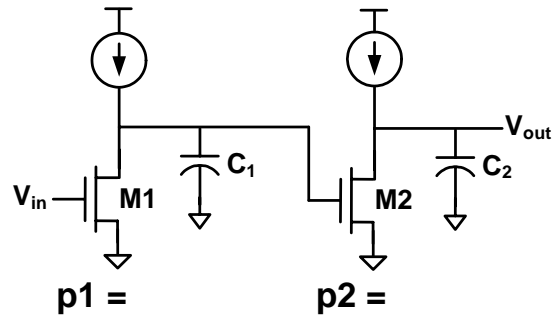

- Two closely spaced poles - is this circuit stable?

2-Stage Stability cont'd


Compensation Techniques

- **Many options – best one depends on situation at hand**
- **Look at a few general categories:**
 - **Narrowbanding**
 - **Wideband input stage (pre-amp)**
 - **Miller**

Narrowbanding


- **Narrowbanding**
 - **Lower one of the poles**
 - **Or introduce a new one**
- **Stability OK, but (feedback) bandwidth low**
 - **Example: offset cancellation**

Pre-amp

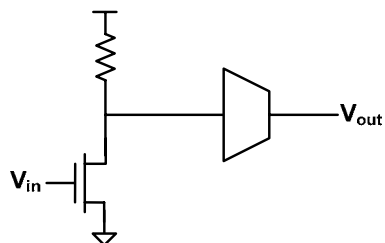

- Build a pre-amp with bandwidth much higher than 2nd stage
 - Usually limits achievable pre-amp gain

Miller Compensation

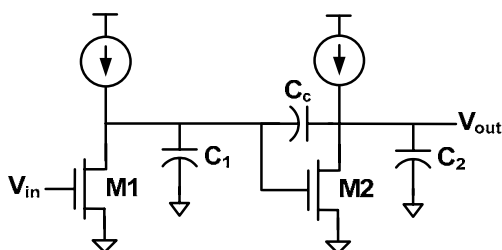

- Very common form of compensation
 - Why is this “pole splitting” good?

Miller Compensated Poles/Zeros

Phase Margin Engineering

$$\omega_u \approx F \frac{g_{m1}}{C_c} \quad |p_2|, z \gg \omega_u \text{ of } T(s)$$

choose $|p_2| \geq K \omega_u$

$$C_c \geq K F C_2 \frac{g_{m1}}{g_{m2}}$$

$$\frac{z}{\omega_u} = \frac{1}{F} \frac{g_{m2}}{g_{m1}}$$

$$\frac{z}{|p_2|} \approx \frac{C_2}{C_c}$$

- Higher K \rightarrow higher C_c

- For fixed C_c , larger $C_L = C_2$ *lowers* phase margin

- Zero can add significant phase lag
 - Unless $g_{m2} \gg F g_{m1}$

Nulling Resistor

$$z \rightarrow \frac{1}{\left(\frac{1}{g_{m2}} - R_z\right)C_c}$$


p_1, p_2 : no change

$$p_3 \approx -\frac{1}{R_z C_1}$$

- **R_z limits feedforward current at high frequency**
 - Pushes feedforward zero to higher frequency
- **Adds new pole p_3**

Nulling Resistor Implementation

Cascode Compensation (Ahuja)

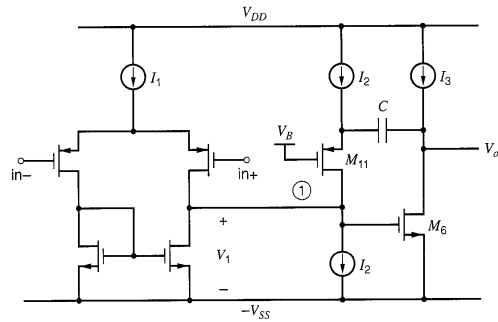

- No RHP zero
- But cost in power can be high
 - (I_2 needs to slew C_c)

Cascode Compensation (Ribner)

Noise Analysis

- Need a simplified model:

Noise Analysis cont'd

$$v_o = \frac{1}{Fg_{m1}} \frac{1}{1 + \frac{s}{\omega_o Q} + \frac{s^2}{\omega_o^2}} \left(i_{n1} - i_{n2} \frac{sC_c}{g_{m2}} \right)$$

with

$$\omega_o^2 = \frac{Fg_{m1}g_{m2}}{C_c(C_c + C_L)}$$

$$\omega_o Q = \frac{Fg_{m1}}{C_c}$$

Total Noise at Output

$$\overline{v_{oT}^2} = \frac{k_B T}{C_c} \frac{\gamma}{F} + \frac{k_B T}{(C_c + C_L)} \gamma$$

$$\overline{v_{oT}^2} = \frac{k_B T}{C_c} \frac{\gamma}{F} \left(1 + \frac{F C_c}{C_c + C_L} \right)$$

- Noise from first stage dominates
- Noise capacitor: **C_c** (NOT C_L!)

2-Stage CMFB

2-Stage CMFB
