

EECS240 – Spring 2010

Lecture 4: Design-Driven Small Signal Models



Elad Alon
Dept. of EECS

Small Signal Model

- Never really changes:

$$i_{ds} = \frac{\partial I_{ds}}{\partial V_{gs}} v_{gs} + \frac{\partial I_{ds}}{\partial V_{bs}} v_{bs} + \frac{\partial I_{ds}}{\partial V_{ds}} v_{ds}$$

$$i_{ds} = g_m V_{gs} + g_{mb} V_{bs} + g_{ds} V_{ds}$$

- Just need to know the coefficients...
 - Look at design-driven methods to figure out what r_o , g_m , etc. are
 - And what values you want to choose for them

EECS240

Lecture 4

4

MOSFET Models for Design


- SPICE (BSIM)
 - For verification
 - Device variations
- Hand analysis
 - Velocity-sat model (good mostly for intuition)
 - Small-signal model
- Challenge
 - How to accurately design when hand analysis models may be way off?

EECS240

Lecture 4

2

Output Resistance r_o

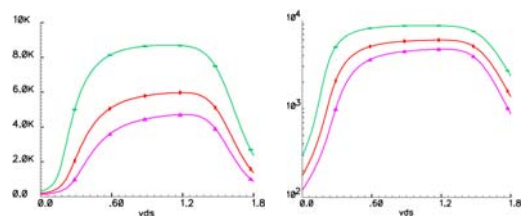

Hopeless to model this with a simple equation
(e.g. $g_{ds} = \lambda I_D$)

EECS240

Lecture 4

5

Parameters Designers Care About


- Layout designer:
 - Mostly care about just W and L
- Circuit designer:
 - Gain $\rightarrow g_m, r_o$
 - Bandwidth $\rightarrow g_m, C_{GS}, C_{GD}, \dots$
 - Power $\rightarrow I_D$
 - Voltage swing \rightarrow minimum V_{DS}
 - Noise
- Can get many of the circuit parameters without resorting to BSIM
 - Or rather, by just using BSIM as a look-up table

EECS240

Lecture 4

3

What You Really Care About: Gain a_{v0}

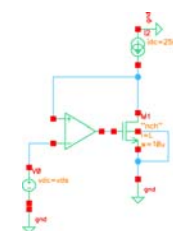


- Represents maximum attainable gain from a transistor
 - Often more useful than r_o
- Simulation Notes:
 - Bias current i_{dc} sets $V_{GS} - V_T$
 - Use feedback to find correct V_{GS} while sweeping V_{DS}
 - Use relatively small gain (100) for fast DC convergence

EECS240

Lecture 4


6

Gain, $a_{v0} = g_m r_o$

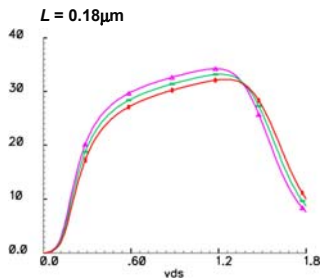


- Strong tradeoff: a_{v0} versus V_{DS} range
- Create plots for several device lengths

Transistor Gain Detail

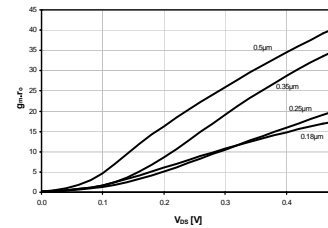

For practical V_{DS} gain penalty is less severe (remember: worst case V_{DS} is what matters!)

Long Channel Gain

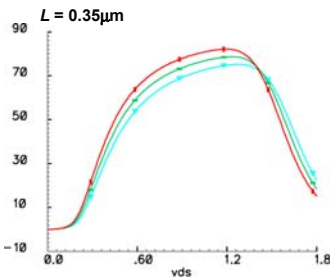

$L \uparrow \rightarrow a_{v0} \uparrow$

g_m : Square Law Model

- In saturation:


$$g_m = \mu C_{ox} \frac{W}{L} \sqrt{\frac{2I_{ds}}{\mu C_{ox} \frac{W}{L}}}$$

$$g_m = \sqrt{2\mu C_{ox} \frac{W}{L} I_{ds}} \propto \sqrt{I_{ds}}$$

$$g_m = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{gs} - V_T)^2 \frac{1}{\frac{1}{2}(V_{gs} - V_T)}$$


$$g_m = \frac{2I_{ds}}{V_{gs} - V_T} = \frac{2I_{ds}}{V_{od}}$$

Technology Trend

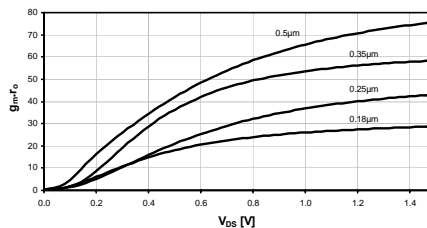

Short channel devices usually have lower peak gain

Figure of Merit: g_m/I_D

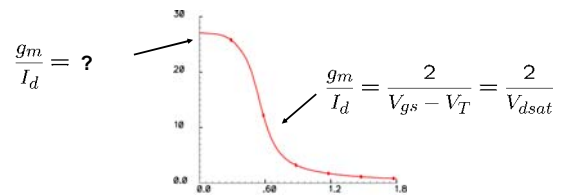

$$\frac{g_m}{I_d} = ?$$

$$\frac{g_m}{I_d} = \frac{2}{V_{gs} - V_T} = \frac{2}{V_{dsat}}$$

- How much g_m per unit current
- Purely a DC metric
 - Will look at dynamic implications later
- Why does g_m/I_D flatten out at low V_{gs} ?

Weak Inversion g_m

- In weak inversion we have bipolar behavior

$$I_{ds} \approx \frac{W}{L} I_{ds,0} e^{\frac{q(V_{gs}-V_T)}{nkT}}$$

$$g_m = \frac{\partial I_{DS}}{\partial V_{GS}} = \frac{\frac{W}{L} I_{ds,0} e^{\frac{q(V_{gs}-V_T)}{nkT}}}{n \frac{kT}{q}}$$

- Good model if transistor is actually used in weak inversion

$$g_m = \frac{I_{DS}}{n \frac{kT}{q}} \propto I_{DS}$$

EECS240

Lecture 4

13

Substitute for g_m/I_D : V^*

- Define:

$$V^* = \frac{2I_D}{g_m} \Leftrightarrow \frac{g_m}{I_D} = \frac{2}{V^*}$$

e.g. $V^* = 200\text{mV} \rightarrow g_m/I_D = 10 \text{ V}^{-1}$

- Square-law devices: $V^* = V_{GS} - V_{TH} = V_{od}$

Square law : $g_m = \frac{2I_D}{V_{GS} - V_{TH}} = \frac{2I_D}{V^*}$


- Remember: real devices do **not** obey the square law!

EECS240

Lecture 4

16

Efficiency g_m/I_D

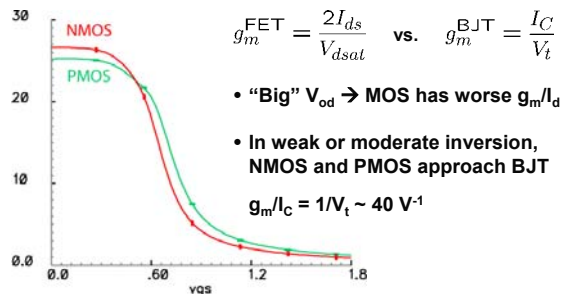

EECS240

Lecture 4

14

V_{od} vs V^*

- | | |
|--|---|
| <ul style="list-style-type: none"> Overdrive voltage V_{od} <ul style="list-style-type: none"> Cannot be measured Complex equations "Long channel" devices: <ul style="list-style-type: none"> $V_{od} = V_{dsat} = V^*$ $I_D \sim V^{*2}$ Boundary between triode and saturation r_o "large" for $V_{DS} > V^*$ C_{GS}, C_{GD} change | <ul style="list-style-type: none"> $V^* = 2I_D/g_m$ <ul style="list-style-type: none"> Measure (simulate) easily Complex equations "Short channel" devices: <ul style="list-style-type: none"> All interpretations of V^* are approximations Except $V^* = 2 I_D / g_m$ (but $V^* \neq V_{dsat}$) |
|--|---|

EECS240

Lecture 4

17

Efficiency as a Design Parameter

- Why not use g_m/I_D for design?
- Can always determine value (from I_D and g_m)
 - Can do this "independently" of short channel effects (using simulator)
- Units (V^{-1}) and physical interpretation a little strange
 - But we'll just redefine things slightly to fix this


EECS240

Lecture 4

15

Design Example

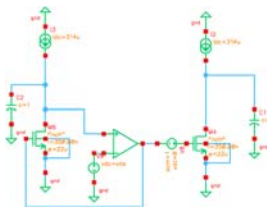Example: Common-source amp
 $a_{v0} > 70$, $f_u = 100\text{MHz}$ for $C_L = 5\text{pF}$



$a_{v0} > 70 \rightarrow L = 0.35\mu\text{m}$

$g_m \approx 2\pi f_u C_L = 3.14\text{mS}$

Pick $V^* = 200\text{mV}$


$I_D = \frac{g_m V^*}{2} = 314\mu\text{A}$

EECS240

Lecture 4

18

Device Sizing

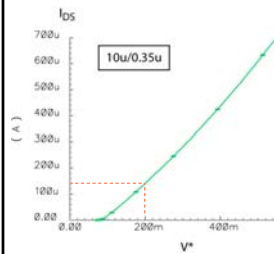


- Pick $L = 0.35\mu\text{m}$
- Pick $V^* = 200\text{mV}$
- Determine $g_m = 3.14\text{mS}$
- $I_D = 0.5 g_m V^* = 314\mu\text{A}$
- W from graph (generate with SPICE)
 - $W = 10\mu\text{m} (314\mu\text{A} / 141\mu\text{A}) = 22\mu\text{m}$
- Create these graphs for several device lengths and flavors

EECS240

Lecture 4

19

PMOS AC Model

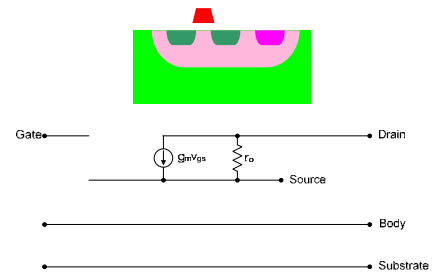


EECS240

Lecture 4

22

Common Source Verification

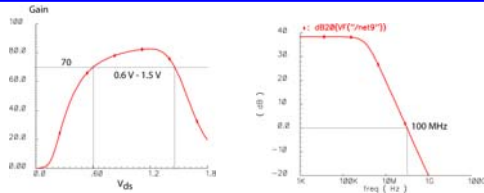

- Amplifier gain > 70; gain-bandwidth “dead on”
- Output range to 0.6V – 1.5V for gain (about $\pm 0.45\text{V}$ swing)
- How did we pick $V^* = 200\text{mV}$? Why not 75mV ?
 - Need to look at AC model...

EECS240

Lecture 4

20

SPICE Charge Model

- Charge conservation
- MOSFET:
 - 4 terminals: S, G, D, B
 - 4 charges: $Q_S + Q_G + Q_D + Q_B = 0$ (3 free variables)
 - 3 independent voltages: V_{GS}, V_{DS}, V_{SB}
 - 9 derivatives: $C_{ij} = dQ_i / dV_j$, e.g. $C_{G,GS} \sim C_{GS}$
 - $C_{ij} \neq C_{ji}$


Ref: HSPICE manual, “Introduction to Transcapacitance”, pp. 15:42, Metasoft, 1996.

EECS240

Lecture 4

23

Small-Signal AC Model

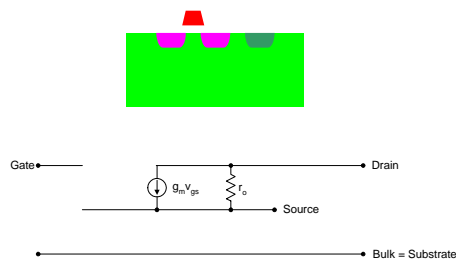

EECS240

Lecture 4

21

Small Signal Capacitances

	Weak inversion	Strong inversion linear	Strong inversion saturation
C_{GS}	C_{ol}	$C_{GC}/2 + C_{ol}$	$2/3 C_{GC} + C_{ol}$
C_{GD}	C_{ol}	$C_{GC}/2 + C_{ol}$	C_{ol}
C_{GB}	$C_{GC} \parallel C_{CB}$	0	0
C_{SB}	C_{JSB}	$C_{JSB} + C_{CB}/2$	$C_{JSB} + 2/3 C_{CB}$
C_{DB}	C_{JDB}	$C_{JDB} + C_{CB}/2$	C_{JDB}

$$C_{GC} = C_{ox} WL$$

$$C_{CB} = \frac{\epsilon_{si}}{x_d} WL$$

0.35u Process

$$C_{ox} = 5.3 \text{ fF}/\mu\text{m}^2$$

$$C_{olN} = 0.24 \text{ fF}/\mu\text{m}$$


$$C_{olP} = 0.48 \text{ fF}/\mu\text{m}$$

EECS240

Lecture 4

24

Layout

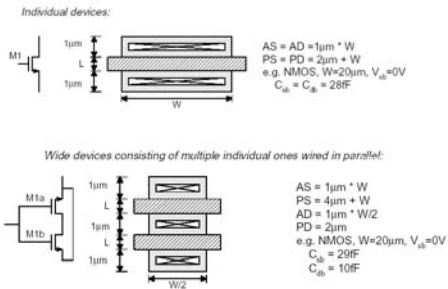


EECS240

Lecture 4

25

Efficiency g_m/I_D versus f_T

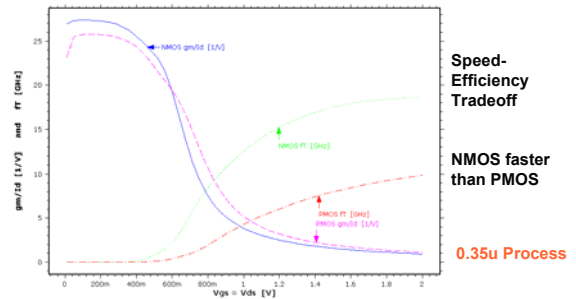

EECS240

Lecture 4

28

Source/drain Parasitics and HSPICE


- ACM=3 model (not in our current library)
 - HDIF = half of heavily doped diffusion length
- GEO = 0: No sharing
- GEO = 1: Drain shared
- GEO = 2: Source shared
- GEO = 3: Both shared

EECS240

Lecture 4

26

Device Scaling

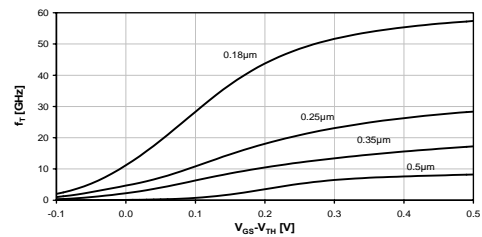

Short channel devices significantly faster

EECS240

Lecture 4

29

Dynamic Figure of Merit

- Unity current-gain bandwidth

$$\omega_T = \frac{g_m}{C_{gs} + C_{gd}}$$

$$\omega_T = \frac{3\mu V_{od}}{2L^2} = \frac{3}{2}\omega_{[]}\quad (\text{Long channel model, } C_{gd}=0)$$

- For degenerate short channel device


$$\omega_T = \frac{3\nu_{sat}}{2L} = \frac{3}{2}\frac{1}{\tau_{sat}}$$

EECS240

Lecture 4

27

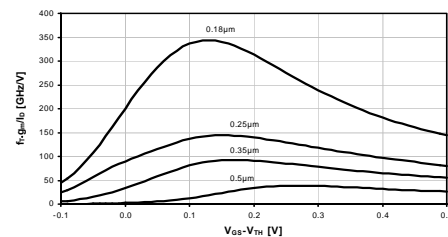Composite Figure-of-Merit: $f_T \cdot g_m/I_D$



Peak performance for low $V_{GS}-V_{TH}$ (implies low V^*)

- Guides choice of V^* : if in doubt,

EECS240

Lecture 4

30

Small Signal Design Summary

- Determine g_m (from design objectives)
- Pick L
 - Short channel \rightarrow high f_T
 - Long channel \rightarrow high r_o , a_{v0} , better matching
- Pick $V^* = 2I_D/g_m$ based on qualitative interpretation
 - Small $V^* \rightarrow$ large signal swing, high current efficiency
 - High $V^* \rightarrow$ high f_T , lower device parasitics
 - Also affects noise (see later)
- Determine I_D (from g_m and V^*)
- Determine W (SPICE / plot) \leftarrow takes care of short channel effects, etc.
- Accurate for short channel devices \rightarrow key for design