


EECS240 – Spring 2010

Lecture 6: Noise Analysis Techniques




Elad Alon
Dept. of EECS

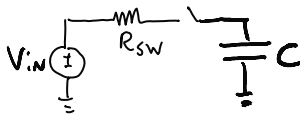Noise Variance in a Real Circuit: Sample and Hold



- Noise on the capacitor:
$$\overline{v_{on}^2(f)} = 4k_B T R \left| \frac{1}{1 + sRC} \right|^2$$
$$\rightarrow \overline{v_{oT}^2} = \int_0^\infty \overline{v_{on}^2(f)} df = \frac{k_B T}{C}$$
- So effective bandwidth is:
$$4k_B T R \Delta f = \frac{k_B T}{C}$$
$$\rightarrow \Delta f = \frac{1}{4RC} = \frac{\pi}{2} f_o$$

SPICE Verification

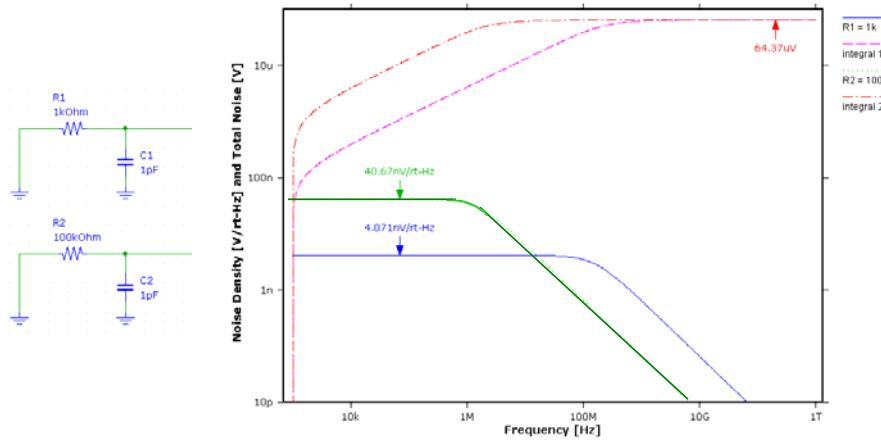

Energy-Based Analysis

Sampled Signal Signal-To-Noise Ratio

- **SNR:** $SNR = \frac{P_{sig}}{P_{noise}}$

- **Signal Power (sinusoidal source):**

$$P_{sig} = \frac{1}{2} V_{zero-peak}^2$$

- **Noise Power (assuming thermal noise dominates):**

$$P_{noise} = \frac{k_B T}{C} n_f$$

- **So:**

$$SNR = \frac{\frac{1}{2} C V_{zero-peak}^2}{n_f k_B T}$$

$$SNR \xrightarrow[\uparrow \times 4]{\downarrow} \uparrow +6dB$$

dB versus Bits

- **Quantization “noise”**

- Quantizer step size: Δ

- Box-car pdf variance: $S_Q = \frac{\Delta^2}{12}$

N	dB
8	50
16	98
24	146

- **SNR of N-Bit sinusoidal signal**

- Signal power $P_{sig} = \frac{1}{2} \left(2^N \frac{\Delta}{2} \right)^2$

- SNR $SNR = \frac{P_{sig}}{S_Q} = 1.5 \times 2^{2N}$

- 6.02 dB per Bit $= [1.76 + 6.02N] \text{ dB}$

SNR versus Power

- 1 Bit \rightarrow 6dB \rightarrow 4x SNR
- 4x SNR \rightarrow 4x C
- Circuit bandwidth $\sim g_m/C \rightarrow$ 4x g_m
- Keeping V^* constant \rightarrow 4x I_D , 4x W
- Thermal noise limited circuit:
 - Each bit QUADRUPLES power!
- Overdesign is expensive
 - Better do the analysis right!
 - Need to know how to get analytical expressions for more general circuits


Important Integrals

$$\int_0^{\infty} \left| \frac{1}{1 + \frac{s}{\omega_o}} \right|^2 df = \frac{\omega_o}{4}$$

$$\int_0^{\infty} \left| \frac{1}{1 + \frac{s}{\omega_o Q} + \frac{s^2}{\omega_o^2}} \right|^2 df = \int_0^{\infty} \left| \frac{\frac{s}{\omega_o}}{1 + \frac{s}{\omega_o Q} + \frac{s^2}{\omega_o^2}} \right|^2 df = \frac{\omega_o Q}{4}$$

$$\int_0^{\infty} \left| \frac{\frac{s}{\omega_z} + 1}{1 + \frac{s}{\omega_o Q} + \frac{s^2}{\omega_o^2}} \right|^2 df = \frac{\omega_o Q}{4} \left(\frac{\omega_o^2}{\omega_z^2} + 1 \right)$$

CS Amplifier

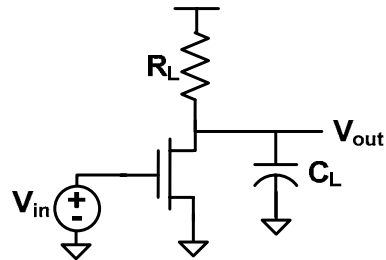


$$\begin{aligned}
 \overline{v_{on}^2(f)} &= 4k_B T \left(\frac{1}{R_L} + \frac{2}{3} g_m \right) \left| \frac{R_L}{1 + sR_L C_L} \right|^2 \\
 \overline{v_{or}^2} &= 4k_B T \left(\frac{1}{R_L} + \frac{2}{3} g_m \right) R_L^2 \int_0^\infty \left| \frac{1}{1 + sR_L C_L} \right|^2 df \\
 &= 4k_B T \left(\frac{1}{R_L} + \frac{2}{3} g_m \right) R_L^2 \frac{1}{4R_L C_L} \\
 &= \frac{k_B T}{C_L} \left(1 + \frac{2}{3} g_m R_L \right) \\
 &= \frac{k_B T}{C_L} \left(1 + \frac{2}{3} |A_{vo}| \right) \\
 &= \frac{k_B T}{C_L} n_F
 \end{aligned}$$

Two-Stage Amplifier


Input Equivalent Noise

Equivalent Noise Generators

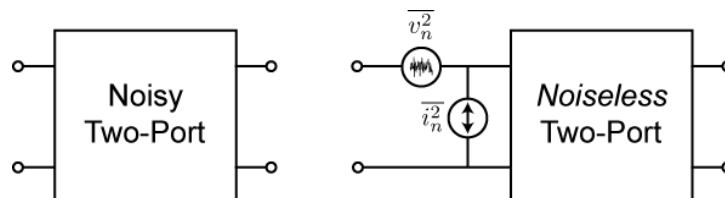


- **Model for noisy two-port:**
 - *Noiseless* two-port
 - Plus equivalent input noise sources
- In general, v_n and i_n are correlated.
 - Ignore that for now

Finding the Equivalent Generators

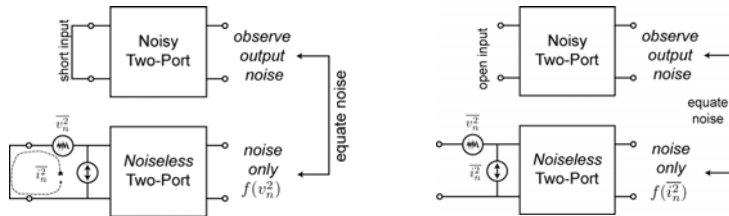


- Find v_n and i_n by opening and shorting the input
- Shorted input:
 - Output noise due only to v_n
- Open input:
 - Output noise due only to i_n

Role of Source Resistance

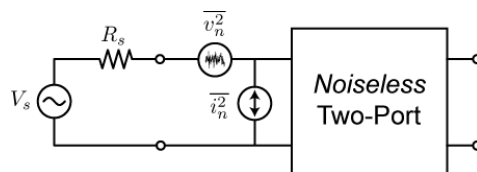

- If R_s is large:
 - Design amplifier with low i_n (MOS)
- If R_s is low:
 - Design amplifier with low v_n (BJT)
- For a given R_s , there is an optimal v_n/i_n ratio
 - Alternatively, for a given amp, there is an optimal R_s

Total Output Noise

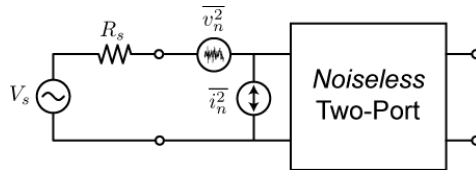

$$\begin{aligned}\overline{v_o^2} &= (\overline{v_n^2} A_v^2 + \overline{v_{R_s}^2} A_v^2) \left(\frac{R_{in}}{R_{in} + R_s} \right)^2 + \left(\frac{R_{in}}{R_{in} + R_s} \right)^2 R_s^2 \overline{i_n^2} A_v^2 \\ &= (\overline{v_n^2} + \overline{i_n^2} R_s^2 + \overline{v_{R_s}^2}) \left(\frac{R_{in}}{R_{in} + R_s} \right)^2 A_v^2\end{aligned}$$


Optimum Source Impedance

- Can use this to optimize source impedance for minimum added noise from two-port (noise figure):

$$R_n \equiv \frac{v_n^2}{4kT\Delta f} \quad G_n \equiv \frac{i_n^2}{4kT\Delta f}$$

$$R_{opt} = \sqrt{\frac{R_n}{G_n}} = \sqrt{\frac{v_n^2}{i_n^2}}$$

Correlated Noise Sources

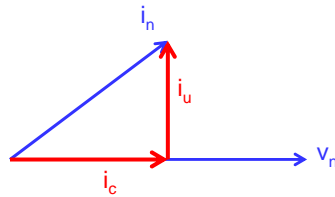


$$i_n = i_c + i_u$$

$$\langle i_u, v_n \rangle = 0$$

$$i_c = Y_C v_n$$

- Partition i_n into two components:
 - Correlated (“parallel”) to v_n
 - Uncorrelated (“perpendicular”) to v_n
- Can use this to re-derive optimum source Z


Loose Ends: Sampled Noise Spectrum

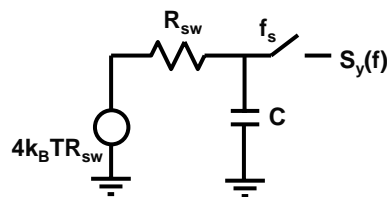

$$S_y(f) = \frac{k_B T_r}{C} \frac{2}{f_s} \frac{1 - e^{-2a}}{1 + e^{-2a} (1 - \cos 2\pi f T)}$$

$$a = \frac{T}{R_{sw} C} = \frac{T}{\tau} \quad \text{and} \quad T = \frac{1}{f_s}$$
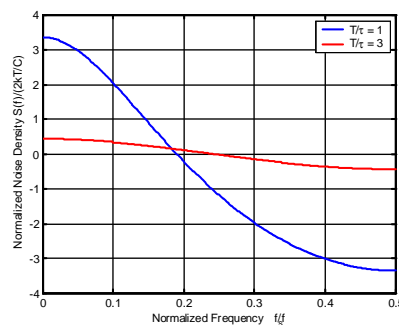
$$\int_0^{f_s/2} S_y(f) df = \frac{k_B T_r}{C}$$




- What if RC doesn't completely settle every cycle?
 - Noise between samples correlated \rightarrow spectrum not white
- If $T/\tau > 3$, correlation small
 - Sampled spectrum white
 - In practice usually the case

Loose Ends: Periodic Noise Analysis

Sampling Noise from SC S/H

Netlist
ahd_include "zoh.def"

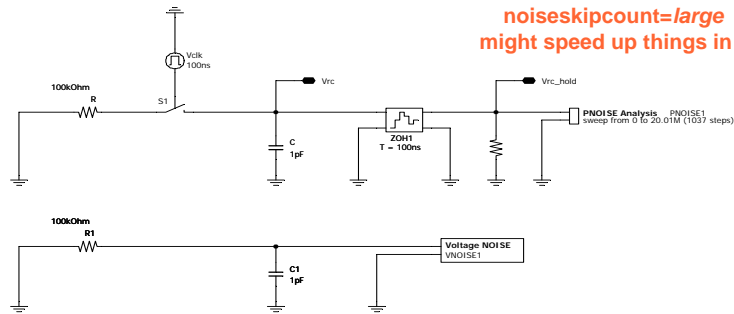Netlist
simOptions options reftol=10u valstol=1n labstol=1p



SpectreRF PNOISE: check
noisetype=timedomain
noisetimepoints=[...]
as alternative to ZOH.
noiseskipcount=*large*
might speed up things in this case.

PSS pss period=100n maxacfreq=1.5G errpreset=conservative
PNOISE (Vrc_hold 0) pnoise start=0 stop=20M lin=500 maxsideband=10